KWAME NKRUMAH UNIVERSITY OF SCIENCE AND TECHNOLOGY

COLLEGE OF ENGINEERING

DEPARTMENT OF ELECTRONIC/ELECTRICAL ENGINEERING



MICROPROCESSOR DESIGN PROJECT
MICROPROCESSORS (COE 381)

GROUP 13

- 1. Emmanuel Kyeremeh 8240519
- 2. Richard Ampofo 8228919
- 3. Benecentia Mafo-Kwofie 8241419
- 4. Brandon Idun-Tawiah 8238419
- 5. Michael Acquah 8225819
- 6. Rina Kusi Gyan 8240119
- 7. Kwesi Asiedu Sarpong 8246419
- 8. Paul Amoah 8228719

ACKNOWLEDGEMENT

We would first of all like to thank the almighty God for taking us through this project. We would also like to thank *Chris Nutsukpui* and *Dr. Jephthah Yankey* for their very much appreciated assistance in the undertaking of this project.

TABLE OF CONTENTS


| 1. | SPECIFICATIONS | 5 |
|----|--|----|
| | 1.1. COMPONENTS USED | 5 |
| | 1.2. MEMORY AND ALU BUS SPECIFICATIONS | 5 |
| 2. | THE ARCHITECTURE AND THE MICROARCHITECTURE | 6 |
| | 2.1. INSTRUCTION CATEGORIES | 6 |
| | 2.2. INSTRUCTION TYPES | 6 |
| | 2.4. MEMORY LABELS | 6 |
| | 2.5. A TYPE INSTRUCTIONS | 7 |
| | 2.5.1. INSTRUCTION FORMAT | 7 |
| | 2.5.2. DATAPATHS | 7 |
| | 2.5.3. TRUTH TABLE | 8 |
| | 2.6. B TYPE INSTRUCTIONS | 8 |
| | 2.6.1. INSTRUCTION FORMAT | 8 |
| | 2.6.2. DATAPATHS | 9 |
| | 2.6.3. TRUTH TABLE | 11 |
| | 2.7. C TYPE INSTRUCTIONS | 11 |
| | 2.7.1. INSTRUCTION FORMAT | 11 |
| | 2.7.2. DATAPATHS | 12 |
| | 2.7.3. TRUTH TABLE | 15 |
| | 2.8. COMBINED DATAPATHS | 15 |
| | 2.9. COMPONENTS BUILT IN LOGISIM | 16 |
| | 2.7.1. REGISTERFILE | 16 |
| | 2.7.2. ALU | 17 |
| | 2.7.3. A TYPE CONTROL UNIT | 18 |
| | 2.7.4. B TYPE CONTROL UNIT | 18 |
| | 2.7.5. C TYPE CONTROL UNIT | 19 |
| | 2.7.6. COMBINED CONTROL UNIT | 19 |
| | 2.7.7. COMPLETE MICROPPOCESSOR CIRCUIT | 20 |

1. SPECIFICATIONS

1.1. COMPONENTS USED


Control Unit
Registerfile
ALU - Adder
- Subtractor
- Multiplier
- Divider
- AND
- OR
- NOT
Instruction Memory
Data Memory
Program Counter
Decoders
Multiplexers
Simple Logic Gates

1.2. MEMORY AND ALU BUS SPECIFICATIONS

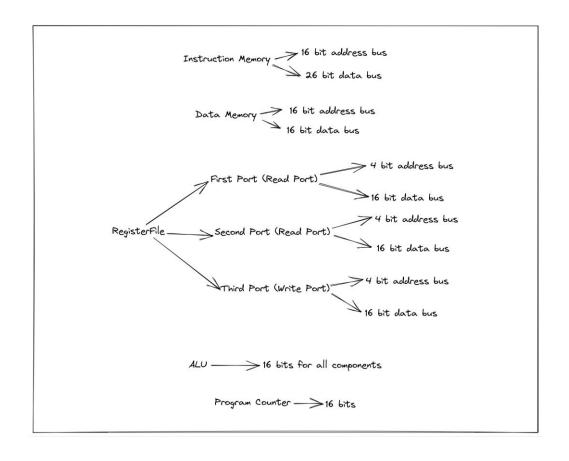


2. THE ARCHITECTURE AND THE MICROARCHITECTURE

2.1. INSTRUCTION CATEGORIES

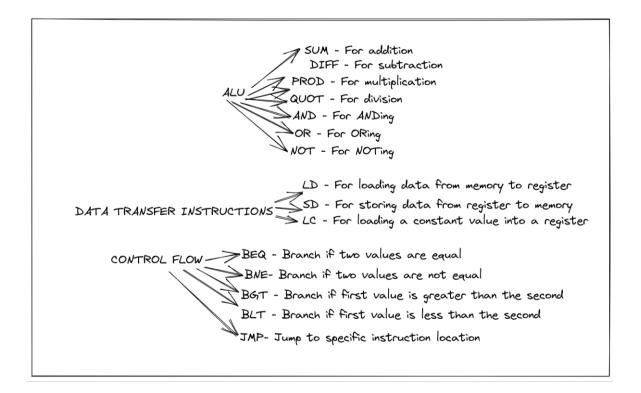

2.2. INSTRUCTION TYPES

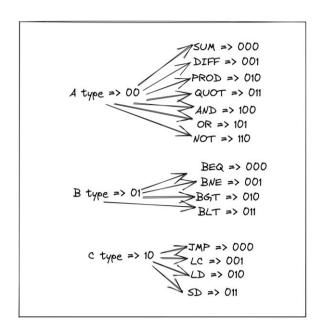



2.4. MEMORY LABELS

| Registers | Data Memory | | | | |
|-----------|-------------|--|--|--|--|
| ~Ο | mO | | | | |
| ď | m1 | | | | |
| • | • | | | | |
| • | • | | | | |
| | • | | | | |
| r15 | m65,535 | | | | |
| | | | | | |


2.5. A TYPE INSTRUCTIONS

2.5.1. INSTRUCTION FORMAT

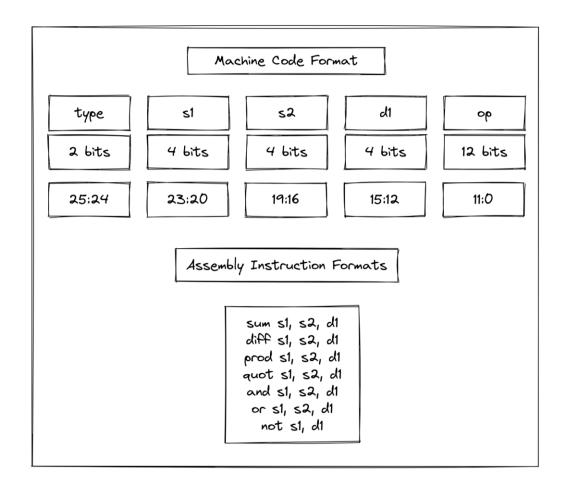

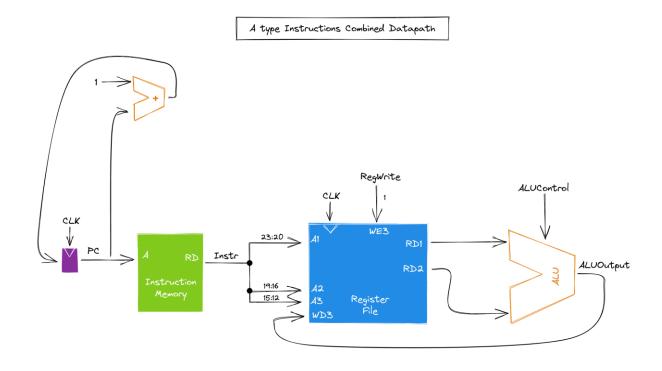


2.5.3. TRUTH TABLE

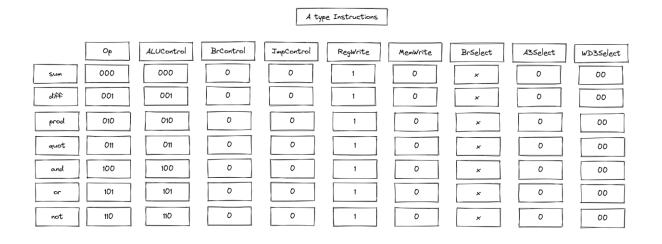


2.6. B TYPE INSTRUCTIONS


2.6.1. INSTRUCTION FORMAT

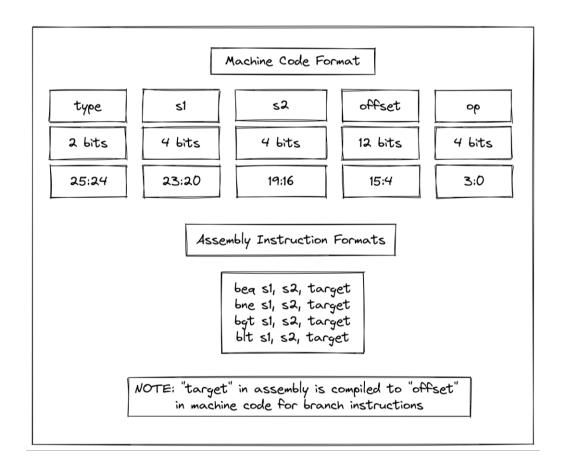


2.6.2. DATAPATHS

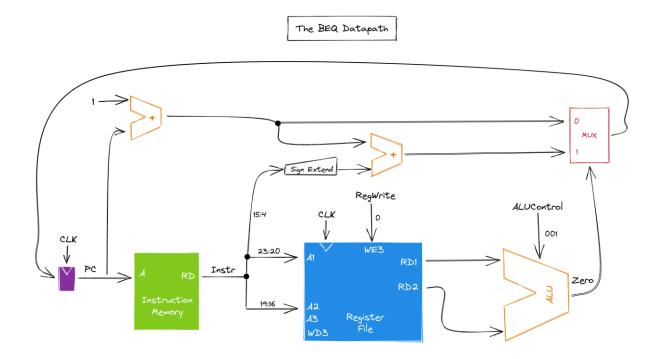


The BNE Datapath

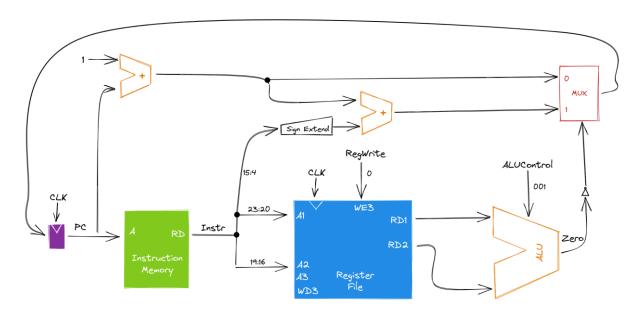


The BGT Datapath

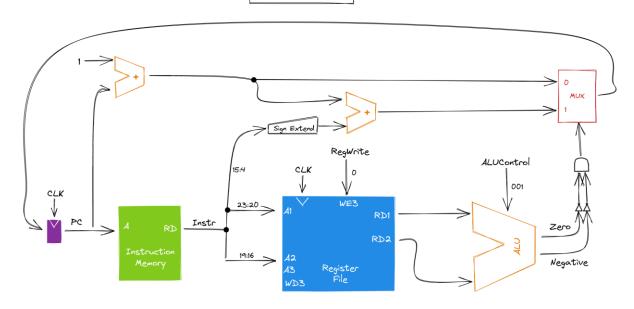

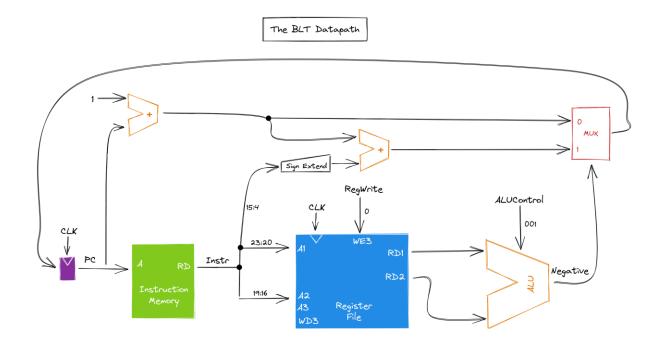


2.6.3. TRUTH TABLE

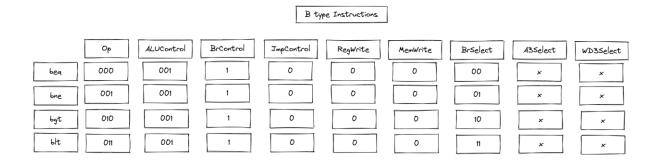



2.7. C TYPE INSTRUCTIONS


2.7.1. INSTRUCTION FORMAT

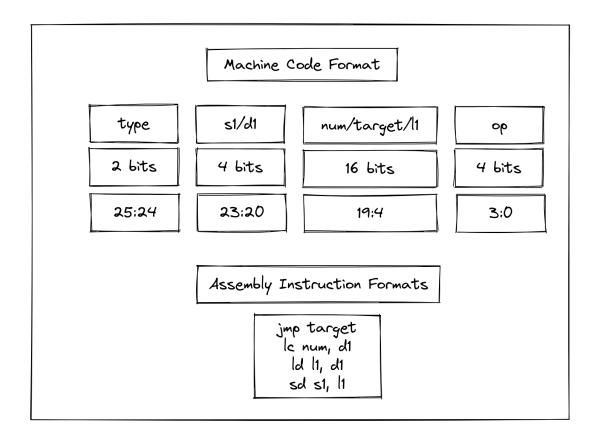


2.7.2. DATAPATHS

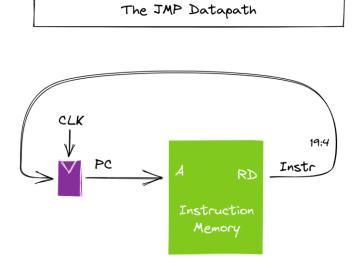


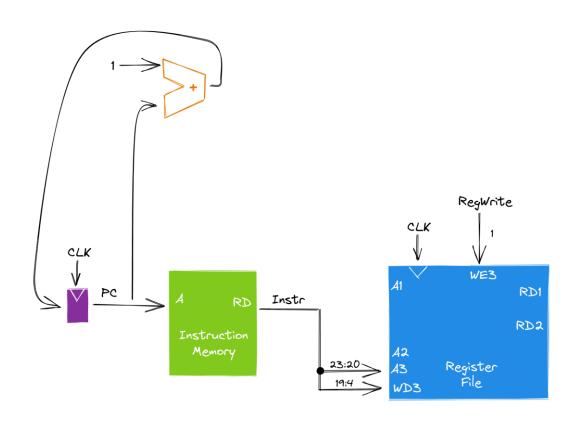

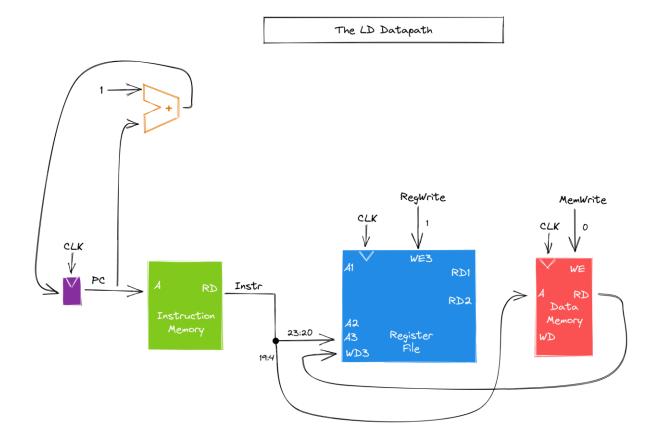

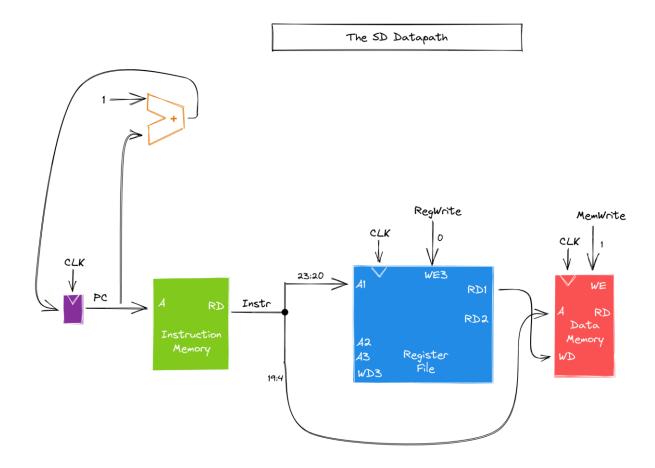


C Type Instructions Combined Datapath

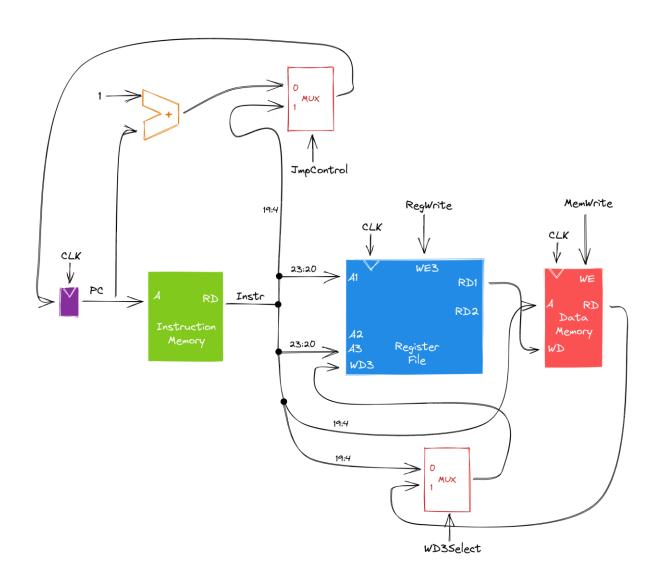

2.7.3. TRUTH TABLE


| | | | | c to | ype Instructions | | | | |
|-----|-----|------------|-----------|------------|------------------|----------|----------|----------|-----------|
| | Ор | ALUCONTrol | BrControl | JmpControl | RegWrite | MemWrite | BrSelect | 43Select | wD3Select |
| jmp | 000 | × | 0 | 1 | 0 | 0 | × | × | × |
| le | 001 | * | 0 | 0 | 1 | 0 | * | 1 | 01 |
| ld | 010 | × | 0 | 0 | 1 | 0 | × | 1 | 10 |
| sd | O11 | × | 0 | 0 | 0 | 1 | × | × | × |

2.8. COMBINED DATAPATHS

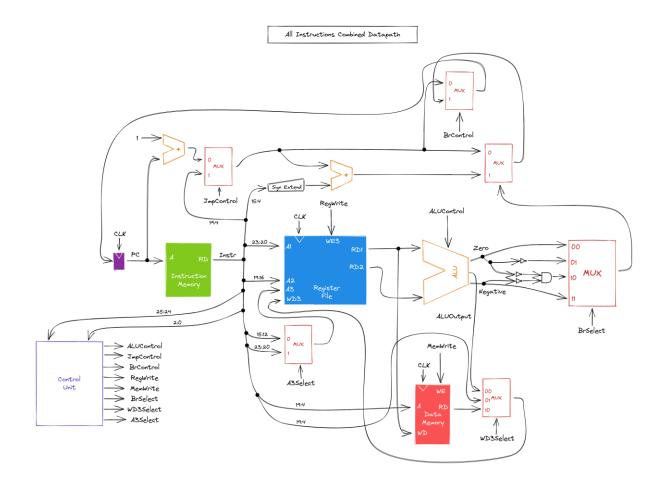


2.9. COMPONENTS BUILT IN LOGISIM


2.7.1. REGISTERFILE

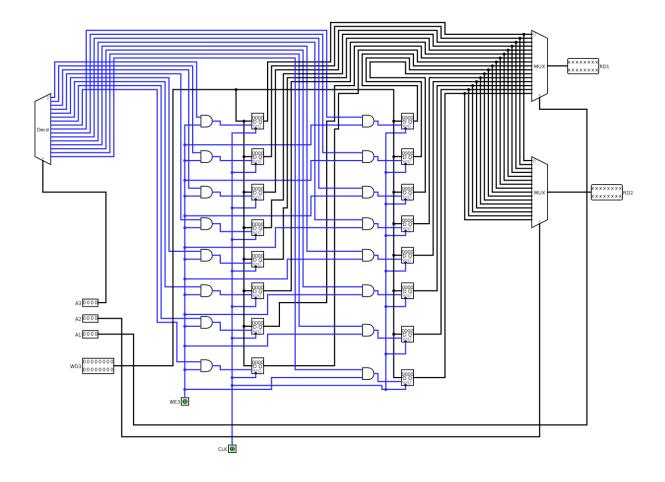


2.7.2. ALU

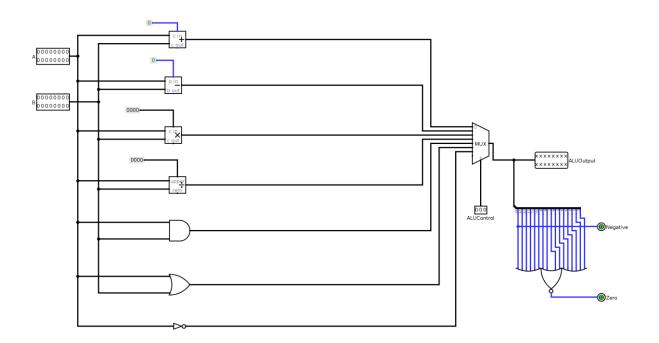


2.7.3. A TYPE CONTROL UNIT

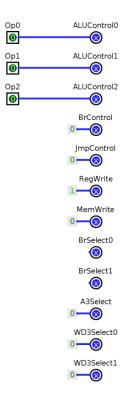


2.7.4. B TYPE CONTROL UNIT

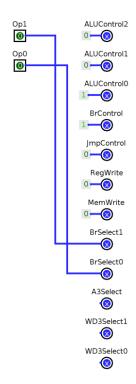

2.7.5. C TYPE CONTROL UNIT

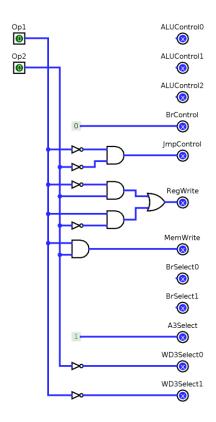

2.7.6. COMBINED CONTROL UNIT

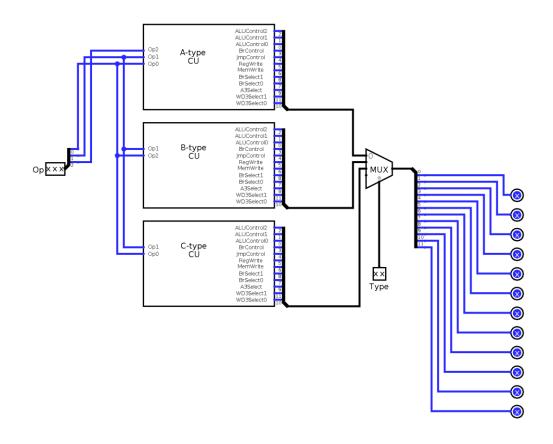

2.7.7. COMPLETE MICROPROCESSOR CIRCUIT

